

Laboratory 8

8. Single-Cycle MIPS CPU Design (5): 16-bits version – One clock cycle per instruction

8.1. Objectives

Study, design, implement and test

- **Memory Unit for the 16-bit Single-Cycle MIPS CPU**
- **Write Back Unit for the 16-bit Single-Cycle MIPS CPU**
- **Other necessary connections for branch / jump address computation**
- **Test the Single-Cycle MIPS CPU**

Familiarize the students with

- Single-Cycle CPU design: Defining the instructions / writing the test program (MIPS assembly language, machine code)
- Xilinx® ISE WebPack
- Digilent Development Boards (**DDB**)
 - [Digilent Basys Board – Reference Manual](#)
 - [Digilent Basys 2 Board – Reference Manual](#)
 - [Digilent Basys 3 Board – Reference Manual](#)

8.2. Reduced Size MIPS Processor Description

(!) Read Lectures 3 and 4 in order to understand the works needed in this laboratory.

Remember that an instruction execution cycle (lecture 4) has the following phases:

- | | | |
|---------|---|------------------------------------|
| • IF | – | Instruction Fetch |
| • ID/OF | – | Instruction Decode / Operand Fetch |
| • EX | – | Execute |
| • MEM | – | Memory |
| • WB | – | Write Back |

Your own Single-Cycle MIPS 16 processor implementation (that you will continue and hopefully finish in this laboratory) will be partitioned in 5 (five) components (new entities). These components will be declared and instantiated in the “test_env” project.

The utility of this implementation will be understood in the future laboratories, when you will implement the pipeline version of your 16-bit MIPS processor!
 In this laboratory you will design, VHDL description, implement and test the Memory Unit, Write Back Unit and the rest of the connections of your own single cycle MIPS 16 processor.

The data-path of the processor (32-bit version), including the control unit and the necessary control signals, is presented in the next figure. In order to reduce the complexity of the data-path, the control signals were not explicitly connected, but rather they can be easily identified by their names.

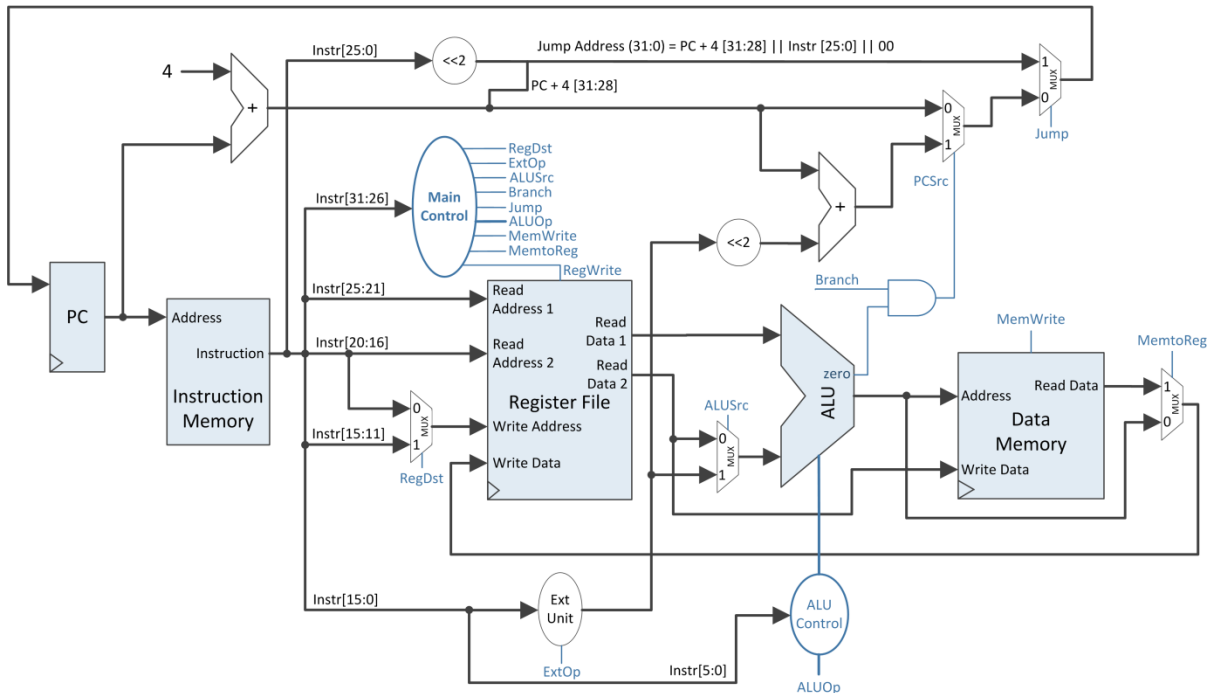


Figure 8-1: MIPS 32 Single-Cycle Data-Path + Control

As a reminder, the instruction formats for your MIPS 16 processor are presented below:

 


Figure 8-2: R-type Instruction format



Figure 8-3: I-type Instruction format



Figure 8-4: J-type Instruction format

The Memory Unit consist in the following component

- Data Memory

The data-path of the Memory Unit is presented in Figure 8-5.

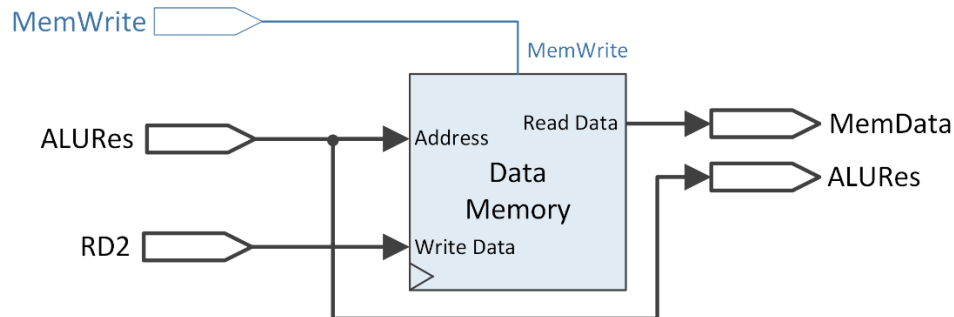


Figure 8-5: Memory Unit Data-Path for MIPS 32

The Data Memory is a RAM with asynchronous read and synchronous write operations. A similar RAM implementation (with synchronous read) was done in laboratory 3.

The inputs of the Memory Unit:

- The clock signal (for the Data Memory Writes)
- 32-bit ALURes signal – consists in the address for the Data Memory
- 32-bit RD2 signal – the second output of the Register File (used only for store word instructions) is the Write Data field for the Data Memory
- MemWrite control signal

The outputs of the Memory Unit:

- 32-bit MemData, the Read Data from the Data Memory (used only for load word instructions).
- 32-bit ALURes, this signal is also the result of the arithmetic-logical instructions that must be stored in Register File, so it is also fed as output for the Memory Unit and input to the Write Back Unit.

The only control signal present in this stage is the MemWrite Control Signal.

- MemWrite = 0 → Nothing is written in the Data Memory.
- MemWrite = 1 → The RD2 signal is written in the Data Memory at the address indicated by the ALURes signal.

The Write Back unit is simply the last multiplexor from Figure 8-1. The rest of the components are the AND gate for generating the PCSrc control signal, the jump address computation.

The control signal for the Write Back multiplexor is MemtoReg and identifies what value is fed to the Write Data port of the Register File in the ID state:

- MemtoReg = 0 → the ALURes signal is the input to the Write Data port of the Register File.
- MemtoReg = 1 → the MemData is the input to the Write Data port of the Register File.

The PCSrc signal identifies if the current instruction is a Branch instruction and if the content of the rs and rt registers are the same; i.e. $RF[rs] == RF[rt]$.

$PCSrc \leftarrow \text{Branch and Zero}$;

8.3. Laboratory Assignments

Read carefully and completely each activity before you begin!

Prerequisites:

- All the assignments from the laboratories 4, 5, 6, 7 completed
- The instruction fetch unit implemented and tested on the Digilent Development Board.
- The instruction decode unit implemented and tested on the Digilent Development Board.
- The instruction execute unit implemented and tested on the Digilent Development Board
- The memory unit implemented and tested on the Digilent Development Board
- Xilinx project with “test_env” including the IF, ID, EX, MEM units (Laboratory 7 Assignment 7.3.3)

Attention: If the homework from the previous laboratories is not completed, you will receive a 1 for this and all future laboratories until the homework is done without the possibility of any corrections to the mark!

8.3.1. Memory Unit Design

Describe a new component (new entity) for the Memory Unit. Use the RAM implementation from laboratory 3 and change the read operation to an asynchronous one. Write only with processes inside the Memory Unit.

Instantiate the Memory Unit in the “test_env” project. Connect all the signals from the Memory Unit in the data-path. The MemWrite signal should be validated with an output of the MPG component as it was previously implemented for the writing in the Register File (RegWrite signal).

8.3.2. Adding the Write Back Unit and the jump address computation

Add the write back multiplexor for your own MIPS processor. Use only one line of code to implement this multiplexor.

Complete your own MIPS processor implementation with the jump address computation and the PCSrc signal computation. Complete all the necessary connections for the data-path as in Figure 8-1 (jump address, branch target address, write back in the register file, etc.).

Test the LW, SW, BEQ and Jump Instructions for your MIPS processor.

8.3.3. Testing it ALL: You own Single-Cycle MIPS 16 processor

At this moment, you should have all the components from the data-path implemented in the “test_env” project.

All the signals present on the data-path must be connecting to the SSD, i.e. the outputs of the IF, ID, EX, M and WB units. Use switches in order to control the display on the SSD (multiplexor):

- $sw(7:5) = 000 \rightarrow$ display the instruction on the SSD
- $sw(7:5) = 001 \rightarrow$ display the next sequential PC (PC + 1 output) on the SSD
- $sw(7:5) = 010 \rightarrow$ display the RD1 signal on the SSD
- $sw(7:5) = 011 \rightarrow$ display the RD2 signal on the SSD
- $sw(7:5) = 100 \rightarrow$ display the Ext_Imm signal on the SSD
- $sw(7:5) = 101 \rightarrow$ display the ALURes signal on the SSD
- $sw(7:5) = 110 \rightarrow$ display the MemData signal on the SSD
- $sw(7:5) = 111 \rightarrow$ display the WD signal on the SSD

On the LEDs, you will display the control signals from the Main Control Unit. You have 8 x 1-bit control signals and ALUOp. Use another switch to control the display on the LEDs:

- $sw(0) = 0 \rightarrow$ Display the 1-bit control signals on the LEDs. The order of the control signals is your own choice.
- $sw(0) = 1 \rightarrow$ Display the n-bit ALUOp signal on the LEDs (the rest of LEDs will have the value '0' for now)

If needed for debugging the processor on the Digilent Development Board you can additionally display other signals on the SSD / LEDs: branch target address, jump address, ALUCtrl, etc.

Now trace your program on the Digilent Development Board instruction by instruction. Be sure that all the control signals / data fields are correct.

Present your Single-Cycle MIPS implementation to your TA.

8.4. References

[1] Computer Architecture Lectures 3 & 4 slides.

- [2] D. A. Patterson, J. L. Hennessy, “Computer Organization and Design: The Hardware/Software Interface”, 5th edition, ed. Morgan–Kaufmann, 2013.
- [3] D. A. Patterson and J. L. Hennessy, “Computer Organization and Design: A Quantitative Approach”, 5th edition, ed. Morgan-Kaufmann, 2011.
- [4] MIPS® Architecture for Programmers, Volume I-A: Introduction to the MIPS32® Architecture, Document Number: MD00082, Revision 5.01, December 15, 2012
- [5] MIPS® Architecture for Programmers Volume II-A: The MIPS32® Instruction Set Manual, Revision 6.02
- [6] MIPS32® Architecture for Programmers Volume IV-a: The MIPS16e™ Application-Specific Extension to the MIPS32™ Architecture, Revision 2.62.
- Chapter 3: The MIPS16e™ Application-Specific Extension to the MIPS32® Architecture.